



EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Quiz II, Semester: Fall 2023

Course: CSE 251 –Electronic Circuits, Section-1
Instructor: Dr. Md. Habibur Rahman, Adjunct Professor, CSE Department
Full Marks: 10 (Will be converted into 5)
Time: 40 Minutes

Note: Answer ALL of the questions. Course outcomes (CO), cognitive levels and marks of each question are mentioned at the right margin.

1. For the given summing amplifier (Fig.1) calculate the output voltage for $v_a = v_b = v_c = 5\text{ V}$. Also calculate the current through all resistors. [CO3, Mark 3]

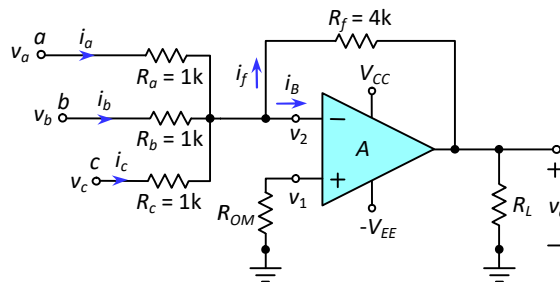


Fig.1: Summing amplifier

2. Analyze the following circuit and determine the output waveform for the given input. Draw the output waveform. Assume $R_1 C_f = 1$ [CO3, Mark: 4]

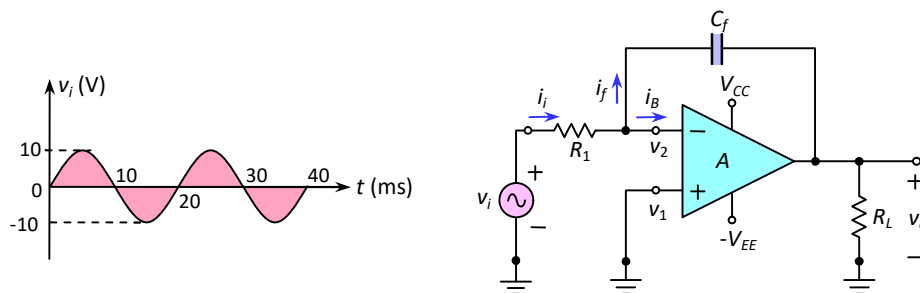


Fig.2: Integrator Circuit

3. For the given transfer characteristics calculate the value of g_m at point A. [CO3, Mark: 3]

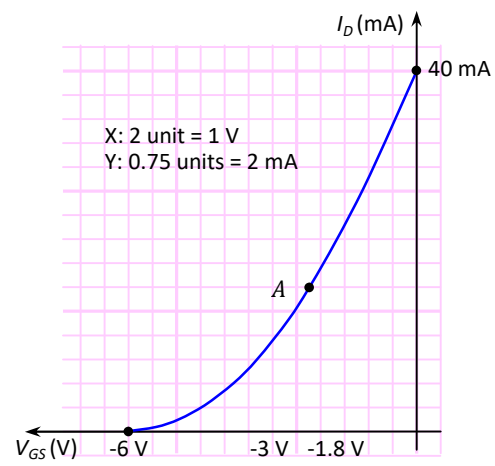


Fig.3: Transfer characteristic curve